

U kolu na slici primenom Kirhofovih zakona pronaći struje  $\underline{I}_1$ ,  $\underline{I}_2$  i  $\underline{I}_3$  poznato je:


$$\underline{Z}_1 = 2 + j3$$

$$\underline{Z}_3 = 2 - j3$$

$$\underline{Z}_2 = 2$$

$$\underline{U}_1 = 84$$

$$\underline{U}_2 = 42$$

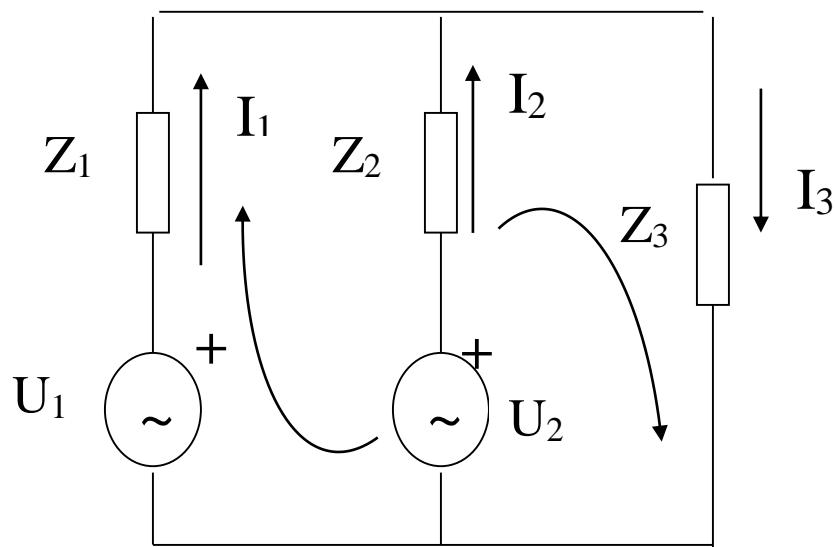

Smerove kontura kao i struja proizvoljno odredujemo.

$$\underline{I}_1 + \underline{I}_2 = \underline{I}_3$$

$$\underline{I}_1 \underline{Z}_1 - \underline{I}_2 \underline{Z}_2 = \underline{U}_1 - \underline{U}_2$$

$$\underline{I}_2 \underline{Z}_2 + \underline{I}_3 \underline{Z}_3 = \underline{U}_2$$


---

$$\underline{I}_1 + \underline{I}_2 = \underline{I}_3$$

struju  $\underline{I}_3$  uvrstićemo u ostale dve

jednačine

$$(2+j3) \underline{I}_1 - 2 \underline{I}_2 = 84 - 42$$

$$2 \underline{I}_2 + (2 - j3) \underline{I}_3 = 42$$


---

$$(2+j3) \underline{I}_1 - 2 \underline{I}_2 = 42 \quad \text{prvu jednačinu prepišemo a drugu sredimo}$$

$$2 \underline{I}_2 + (2 - j3) (\underline{I}_1 + \underline{I}_2) = 42$$


---

$$(2+j3) \underline{I}_1 - 2 \underline{I}_2 = 42$$

$$2 \underline{I_2} + (2 - j3) \underline{I_1} + (2 - j3) \underline{I_2} = 42$$

$$(2 + j3) \underline{I_1} - 2 \underline{I_2} = 42$$

$$(2 - j3) \underline{I_1} + (2 + 2 - j3) \underline{I_2} = 42$$

---

$$(2 + j3) \underline{I_1} - 2 \underline{I_2} = 42 \quad / * (4 - j3)$$

$$(2 - j3) \underline{I_1} + (4 - j3) \underline{I_2} = 42 \quad / * 2$$

---

$$(4 - j3) * (2 + j3) \underline{I_1} - 2 * (\cancel{4 - j3}) \underline{I_2} = 42 * (4 - j3)$$

$$\underline{2 * (2 - j3) \underline{I_1} + 2 * (\cancel{4 - j3}) \underline{I_2} = 42 * 2} \quad \text{sada saberemo}$$

jednačine

$$\underline{I_1} * 2 * (2 - j3) + (2 + j3) * (4 - j3) \underline{I_1} = 42 * (4 - j3) + 84$$

$$\underline{I_1} (4 - j6 + 8 - j6 + j12 + 9) = 42(2 + 4 - j3)$$

$$\underline{I_1} * 21 = 42(6 - j3)$$

$$\underline{I_1} * 21 = 42(6 - j3) / :21$$

$$\underline{I_1} = 2 * (6 - j3)$$

$\underline{I_1} = 12 - j6$

$$(2 + j3) \underline{I_1} - 2 \underline{I_2} = 42$$

$$(2 + j3)(12 - j6) - 2 \underline{I_2} = 42$$

$$24 - j12 + j36 + 18 - 2\underline{I}_2 = 42$$

$$- 2\underline{I}_2 + 42 + j24 = 42$$

$$- 2\underline{I}_2 = -j24$$

$$\boxed{\underline{I}_2 = j12}$$

$$\underline{I}_1 + \underline{I}_2 = \underline{I}_3$$

$$\underline{I}_3 = 12 - j6 + j12$$

$$\boxed{\underline{I}_3 = 12 + j6}$$